

Science

Ohm's Law Word Problems

Ohm's law says that in an [electrical circuit](#), the [current](#) passing through a [resistor](#) between two points, is related to the [voltage](#) difference between the two points, and inversely related to the [electrical resistance](#) between the two points. This relation is shown in the following formula:

$$R = \frac{V}{I}$$

where I is the current in [amperes](#), V is the potential difference in [volts](#), and R is a constant, measured in [ohms](#), called the [resistance](#).

It also says that current is directly proportional to voltage loss through a resistor. That is if current doubles then so does voltage. To make a current flow through a resistance there must be a voltage across that resistance. Ohm's Law shows the relationship between the voltage (V), current (I) and resistance (R). It can be written in three ways:

$$I = \frac{V}{R} \quad \text{or} \quad V = IR \quad \text{or} \quad R = \frac{V}{I}$$

Directions: For each word problem, write an equation. Show your work and solve the equation.

Example:

If a light bulb uses 2 Amps of current at a voltage of 120 volts, what the resistance value?

$$R = \frac{V}{I}$$

$$R = \frac{120}{2}$$

$$R = 60$$

The resistance value is 60 ohms.

1) An electric doorbell operates at 12 volts and has a resistance value of 12 ohms. How much current will the doorbell draw?

Science

Ohm's Law Word Problems continued

2) A small flashlight draws 0.5 Amps at 6 Ohms of resistance. How many volts will the batteries need to supply?

3) We need to construct a circuit to power a red LED lamp. The LED uses 2 volts and draws 1 AMP of current. What value resistor will need to be in the circuit?